

Tentti: 07.11.2008

Nimi: _____

Opiskelijakortin numero: _____

Assignment 1

Analyse the operation of the following combinational logic.

a) present the logic function of F as a minimized sum of products

b) present the logic function of F as a minimized product of sums

c) present the Karnaugh map of F


d) if only variables A, B and C are the inputs of the logic, and the complements \bar{A} , \bar{B} ja \bar{C} must be done separately with NOT-gates, is the presented logic diagram the most simplified realization for this logic function based on the number of transistor switches?

EXPLAIN!

- n-input NAND- or NOR-gate = $2n$ transistors

- n-input AND- or OR-gate = $2n+2$ transistors

- NOT-gate = 2 transistors

 


Assignment 2

a) simulate the following state machine for ten clock cycles. The state machine is initialized to state ABC = 100. Present the simulation result for example as a table, in which the rows represent the clock cycles and the columns are the states of the flip-flops (ABC).

b) how many states does the state machine normally have?

 c) what happens if the state machine goes to the state ABC = 000? **EXPLAIN!**

This is a LFSR (Linear Feedback Shift Register).



Alkutila (ABC) = 100

Initial state (ABC) = 100

Tentti: 07.11.2008

Nimi: _____

Opiskelijakortin numero: _____

Assignment 3

This assignment deals with the operation of the *Arithmetic Logic Unit = ALU*. The operation of the ALU has been defined with symbols and VHDL-code. Your task is to fill in the simulation table below. Write into the table the values of the signal nodes as hexadecimal numbers. Assume, that numbers A and B are in 2's complement format.

<pre> Library ieee; Use ieee.std_logic_1164.ALL; Use ieee.std_logic_unsigned.ALL; ENTITY alu IS PORT(s : IN STD_LOGIC_VECTOR(2 DOWNTO 0); A,B :IN STD_LOGIC_VECTOR(3 DOWNTO 0); F : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)); END alu; ARCHITECTURE Behavior OF alu is BEGIN PROCESS(s,A,B) CASE s IS WHEN "000" => F <= "0000"; WHEN "001" => F <= B - A; WHEN "010" => F <= A - B; WHEN "011" => F <= A + B; WHEN "100" => F <= A XOR B; WHEN "101" => F <= A OR B; WHEN "110" => F <= A AND B; WHEN OTHERS => F <= A"1111"; END CASE; END PROCESS; END Behavior; </pre>	
---	--

s	0	1	2	3	4	5	6	7
A	1	1	5	3	B	D	A	A
B	F	F	7	2	C	4	C	3
ab1								
ab2								
ab3								
ab4								
ab5								
ab6								
F								

Tentti: 07.11.2008

Nimi: _____

Opiskelijakortin numero: _____

Assignment 4

This assignment deals with a digital thermometer. The meter converts the measured temperature (point 1.) between $-30\text{ }^{\circ}\text{C}$... $+30\text{ }^{\circ}\text{C}$ to a voltage between 0.00 V ... 5.00 V (point 2.)

As a result of a measurement the signal level at point 6 corresponds to binary value '1'. Values at points 4 and 5 corresponds to BCD coded binary vectors "0010" and "1001", respectively. What digital or analogue signal values have to exist at points 1., 2., 3., 7. and 8 and what can be seen on the display? Binary vector at point 3 could be encoded to a sign-magnitude or 2's complement form. Give the both options in your answer.

