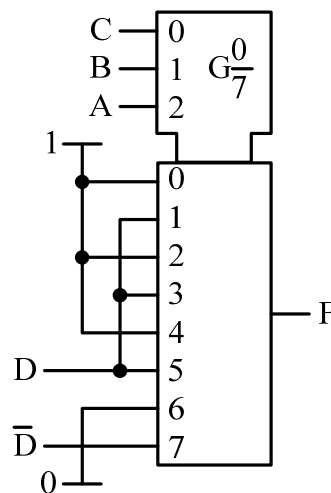




1. a) Present the binary number representing the decimal number -22 as an 8-bit two's complement binary number. Please explain!
- b) if the 6-bit binary number 100111 is said to be in signed magnitude format, what is the absolute value of that binary number as a decimal number? Please explain!
- c) if the hexadecimal number 96 is said to represent an 8-bit two's complement binary number, what is the absolute value of that binary number as a decimal number. Please explain!
- d) how many bits are needed to present the decimal number from 0 to 999 as binary coded decimal numbers (BCD)? Please explain!
- e) how binary numbers and digital logic are related to each other?
- f) how many different truth tables can be presented with three logic variables? Please explain!


2. Analyse the following digital logic. One of the variables (D) of the logic function $F(A,B,C,D)$ is connected to some of the data inputs of the 8:1 multiplexer (MUX), and the rest of the variables are connected to the select inputs of the MUX. Present:

- a) the logic function of F representing the logic diagram without any minimisation
- b) Karnaugh map of F
- c) logic function of F as minimised **product of sums**
- d) logic function of F as minimised **sum of products**



3. Analyse the following NOR-logic. One input is connected to a logic zero. Present:

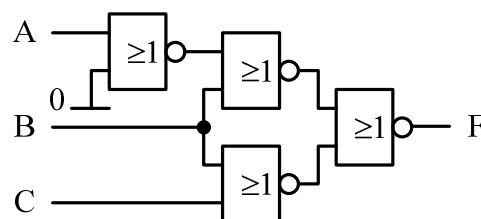- a) identically behaving logic using only 2-input NAND-gates
- b) Karnaugh map of F
- c) logic function of F as minimised **product of sums**





4. How would you realise the following operations related to synchronous logic? Assume that all flip-flops are clocked continuously with a common clock signal. You can draw a picture and explain in writing.

- a) the content of a D-flip-flop must be zeroed synchronously with a certain clock edge, otherwise the next state of the D-flip-flop is determined by the next state decoding logic
- b) a new value must be synchronously loaded to a D-flip-flop with a certain clock edge, otherwise the state of the D-flip-flop remains the same
- c) an asynchronous input signal must be reliably synchronised to the clock signal so, that a pulse with a width of one clock cycle is generated each time the input signal changes its state
- d) what is the difference between combinational logic and sequential logic (state machines)?

5. Analyse the operation of the following logic. Input signal X is synchronous with respect to the clock signal.

- a) fill in the timing diagram by adding to the waveforms the outputs of all flip-flops and the output signal Y
- b) to what characteristics of a D-flip-flop is the operation of the logic based on? Note: all flip-flops receive the clock signal at the same time.
- c) fill in the sentence describing the behaviour of the logic:
 "The logic recognises _____ logic ones in the input signal X"

