

Principles of Electronics Design 521431A

Exam 06/16/2007

1. Assume that the operational amplifier (OPA) shown in figure 1 is ideal and $R_1 = 2 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, $C_1 = 1 \text{ }\mu\text{F}$, $C_2 = 10 \text{ nF}$.
 - (a) What is the output impedance of an ideal OPA?
 - (b) What is the gain u_o/u_i ?
 - (c) What is the overall gain in decibels if there is a -6 dB attenuator after OPA?
 - (d) Does the capacitor C_2 cause a lower or higher corner frequency?
 - (e) What is the input impedance of the configuration?
 - (f) How is it possible to make a non-inverting configuration from the configuration of figure 1?

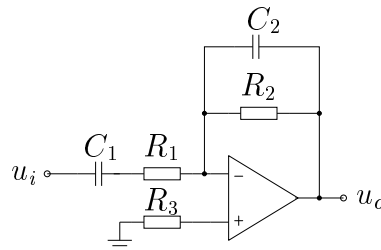


Figure 1: Figure for question 1.

2. What is the input and output impedance of the MOSFET amplifier in figure 2? Select the resistance R_1 and W/L ratio so that the gain $u_L/u_{src} > 10$. Transistor parameters: $\mu_n C_{ox} = 25 \text{ uA/V}^2$, $\lambda = 0$ and $U_t = 2 \text{ V}$. Capacitors C_1 , C_2 and C_3 are high capacitance coupling capacitors. (6p)

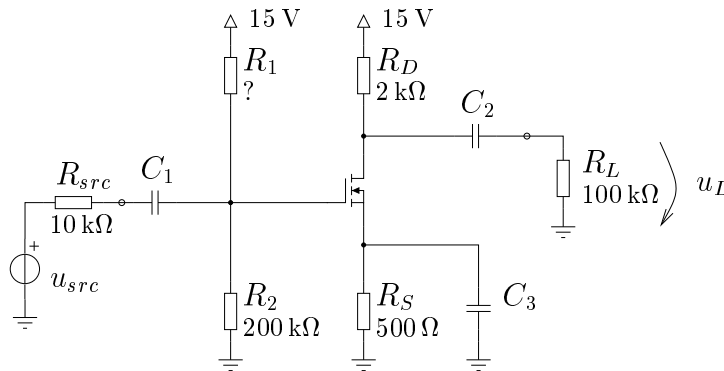


Figure 2: Figure for question 2.

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (u_{GS} - U_t)^2 (1 + \lambda \cdot u_{DS})$$

$$g_m = \left. \frac{\partial i_D}{\partial u_{GS}} \right|_{u_{GS}=U_{GS}} = \mu_n C_{ox} \frac{W}{L} (U_{GS} - U_t)$$

3. (a) Explain the basic structure of a BJ transistor. (1p)
 - (b) What are the operating regions of a BJT and how are they utilized? (1p)
 - (c) The basic laws and equations between the terminal currents and voltages of a BJT in the active region. (2p)
 - (d) How does a BJT create gain in a circuit? (2p)
4. Draw the signals at nodes (1)-(10) shown in figure 3. The diode may be assumed ideal. (6p)

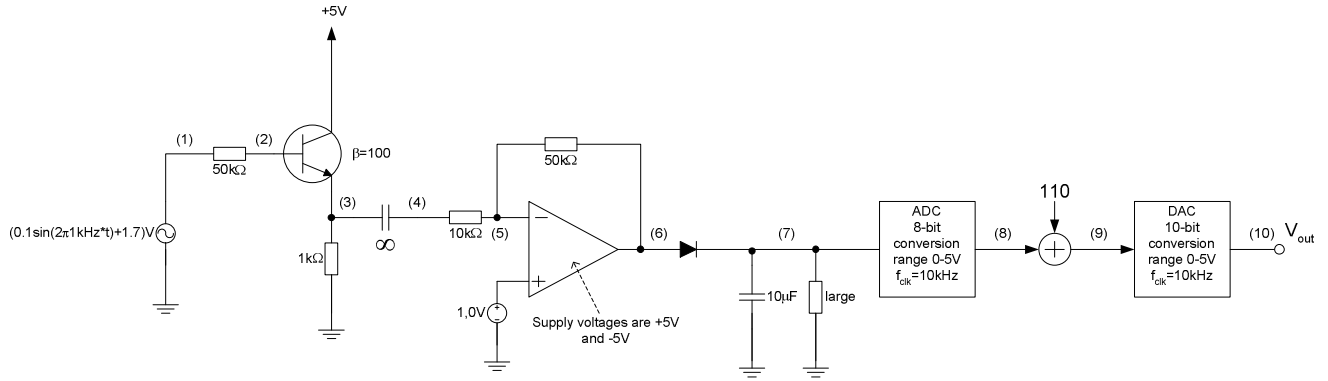


Figure 3: Figure for problem 4.