

Principles of Electronics Design 521431A

Exam 03/27/2009

—

1. (a) For the circuits in figures 1 b), c) and d) sketch the output for the input shown in figure 1 a). (4p)
- (b) What is the output of the circuit shown in figure 1 e) if the input is $u_i = 10 \sin(2\pi ft)$ mV? (2p)

Assume that each diode has a 0.7 V drop when conducting.

2. The MOSFET in the circuit of figure 2 has $\mu_n C_{ox} = 25 \text{ uA/V}^2$, $\lambda = 0$, $W/L = 100$ and $U_t = 2 \text{ V}$. Capacitors C_1 , C_2 and C_3 are large coupling capacitors.
 - (a) Find the values of I_D and g_m at the bias point. (2p)
 - (b) Draw a small-signal equivalent circuit for the circuit. (1p)
 - (c) Find the input and output resistances. (1p)
 - (d) Find the gain u_L/u_{src} . (2p)

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (u_{GS} - U_t)^2 (1 + \lambda \cdot u_{DS})$$

$$g_m = \left. \frac{\partial i_D}{\partial u_{GS}} \right|_{u_{GS}=U_{GS}} = \mu_n C_{ox} \frac{W}{L} (U_{GS} - U_t)$$

3. (a) Calculate the input impedance and voltage gain for the circuit presented in Fig. 3 a), $\beta = 100$. (3p)
- (b) Calculate the output voltage of the circuit presented in Fig. 3 b), as the $R_2 = R_4 = 10 \text{ k}\Omega$, $R_1 = R_3 = 2,5 \text{ k}\Omega$, $u_1 = 1 \text{ V}$ and $u_2 = 2 \text{ V}$ (1p)
- (c) Design an inverting amplifier, which has very large input impedance and gain of -10 using operational amplifiers and resistors. (2p)
4. (a) Draw the schematic diagram of a CMOS inverter and the $V_{IN} - V_{OUT}$ curve of the circuit. (2p)
- (b) What is the advantage of a CMOS switch compared to a switch using one MOS transistor? (1p)
- (c) What is the principle for calculating the dimensions of the transistors in the general structure CMOS logic gate presented in Fig. 4? (1p)
- (d) What is the purpose of the S/H circuit in A/D converters? (2p)

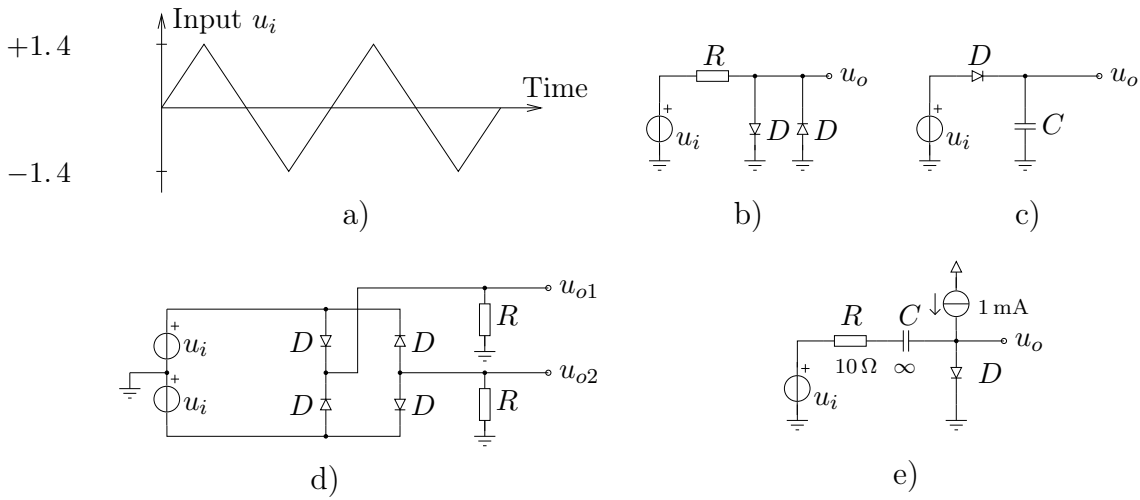


Figure 1: Figure for question 1.

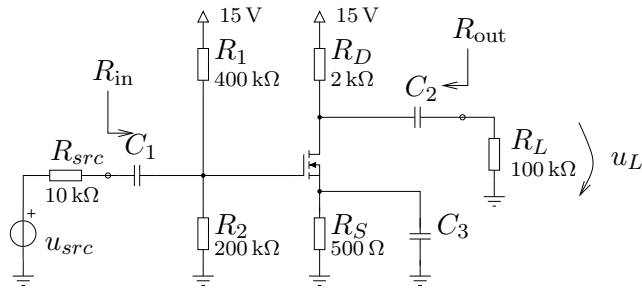


Figure 2: Figure for question 2.

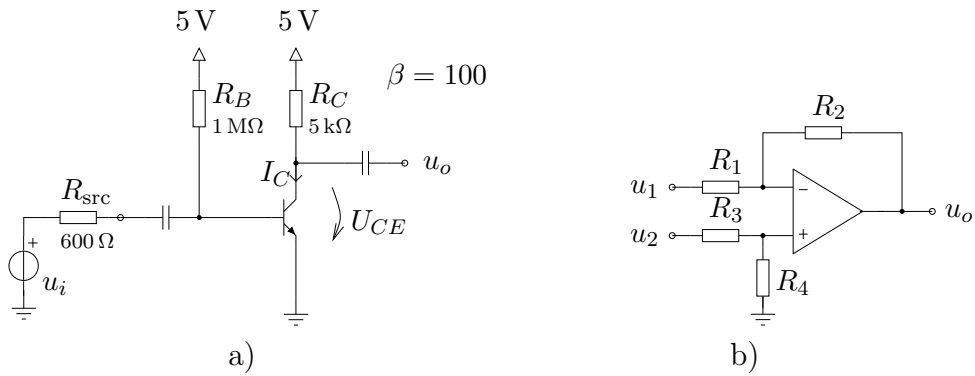


Figure 3: Figures for question 3.

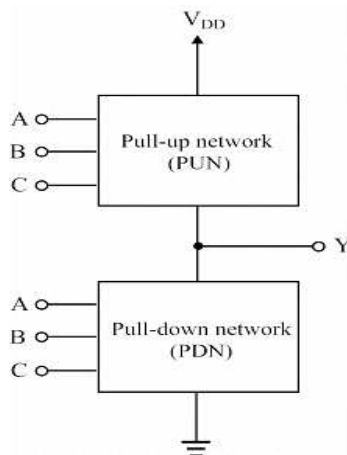


Figure 4: Figure for question 4.