

## Principles of Electronics Design

**Summer exam 29.6.2013**

- Fig. 1 shows the schematic of a NMOS current mirror. Size the resistor  $R_{in}$  (3p) and the width-to-length ratio of a NMOS-transistor  $M_2$  (2p) so, that the current through NMOS-transistor  $M_1$  is  $50 \mu\text{A}$  and the output current  $I_{out} = 300 \mu\text{A}$ . How large is the output resistance of the current mirror (1p)? All the transistors are in the active region and  $\lambda_N = 0$ . Table 1 shows the process parameters of MOS-transistors.(6p)

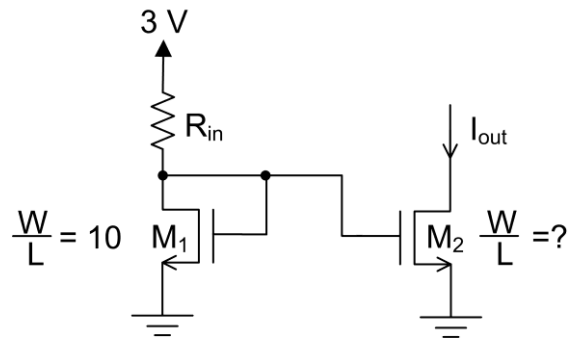


Fig. 1.

- Calculate the DC operation point of amplifier shown in Fig. 2 (2p) (You can assume that  $\beta = \infty$ ). Calculate the amplification  $v_{out}/v_s$  and the input and output impedances  $R_{in}$  and  $R_{out}$  at the signal band (3p).  $\beta=100$  and  $V_{BE} = 0,7 \text{ V}$  when a transistor is conducting. Calculate the maximum input amplitude of the  $v_s$ , which gives the pure, uncut amplitude of the output signal  $v_{out}$  (1p)? Capacitor  $C$  is AC coupling capacitance (short circuit at the band). The saturation voltage of the transistor  $V_{CE-sat} = 0\text{V}$ .(6p)

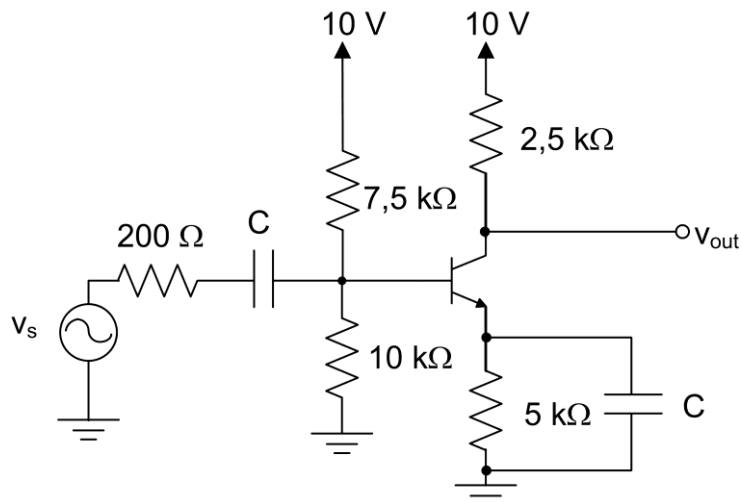


Fig. 2.

3. Write an essay with the following title – *The electrical properties of a diode and the small-signal analysis of a single diode circuit.* (6p)

4. Draw the signals in nodes (1)-(7) marked in Fig. 3. The diode can be assumed ideal. (6p)

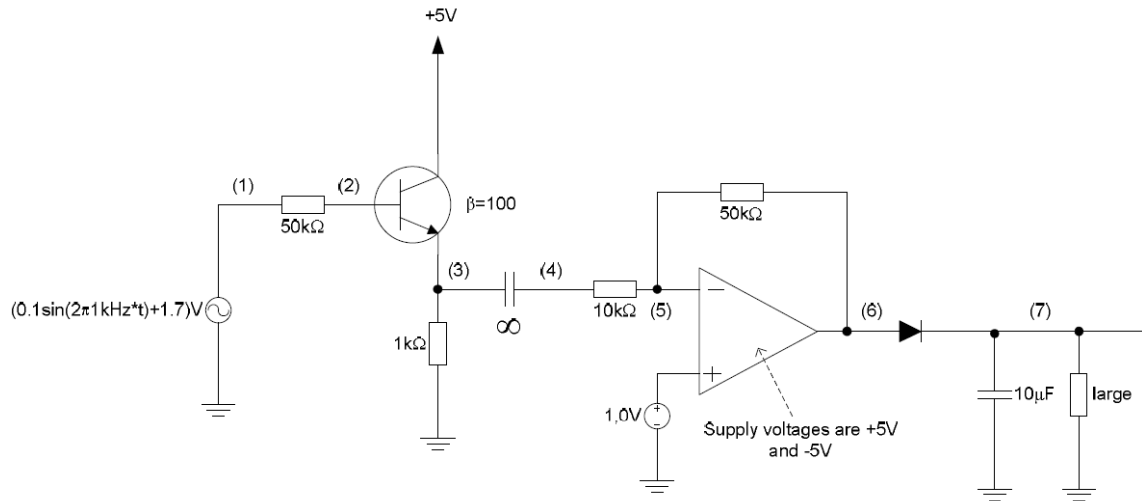


Fig. 3.

Table 1. Process parameters of MOS-transistor.

Type	$V_{TH}$	$\mu C_{ox}$
NMOS	0,5 V	$100 \mu\text{A}/\text{V}^2$
PMOS	-0,5 V	$50 \mu\text{A}/\text{V}^2$

Formulas:

$$\text{NMOS: } i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_{TH})^2$$

$$\text{BJT: } i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right), r_E = \frac{V_T}{I_C} \approx \frac{25 \text{ mV}}{I_C}$$