

Principles of Electronics Design summer exam 27.6.2015

1. Explain shortly question shown below. Pictures can be used to clarify the answers.
 - a) What are the input and output resistances of a current amplifier (I_{out}/I_{in})?(2p)
 - b) What are total impedances of parallel connected capacitance $C = 1 \text{ nF}$ and resistance $R = 1000 \text{ } \Omega$ at the frequencies 0 Hz and $\infty \text{ Hz}$?(2p)
 - c) At the input of an amplifier has the signal of $10\text{mV} \cdot \sin(2\pi ft)$ and you want to get the signal of $150\text{mV} \cdot \cos(2\pi ft)$ at the output. What should be the gain?(2p)
2. Derive the output voltages of operational amplifiers (v_o) shown in figure 1 a) ja b) (4p). Draw the output voltage of the operational amplifier (V_{outc}) shown in figure 1 c) as a function of time when the signal at the input $V_{in} = 0,5 \cdot \sin(2 \cdot \pi \cdot 1\text{kHz} \cdot t)$.(2p) Operational amplifiers are ideal.
3. a) Draw the output voltage V_{out} of the circuit in figure 2 using the small signal model of the diode. (3p)
 - b) Draw the schematic of a diode-based half-wave rectifier and explain how the circuit operates. (3p)
4. Design a common emitter amplifier inside the empty box in figure 3. The input signal is $V_s(t)$ and the output signal is V_o . The gain should be 10 as accurately as possible. The amplitude of $V_s(t)$ is about 10 mV, the frequency is $> 0 \text{ Hz}$ and its DC component is 0 V. You may use a +20 V DC power supply, resistors, capacitors, diodes and NPN-type BJTs (bipolar junction transistors). (6p)

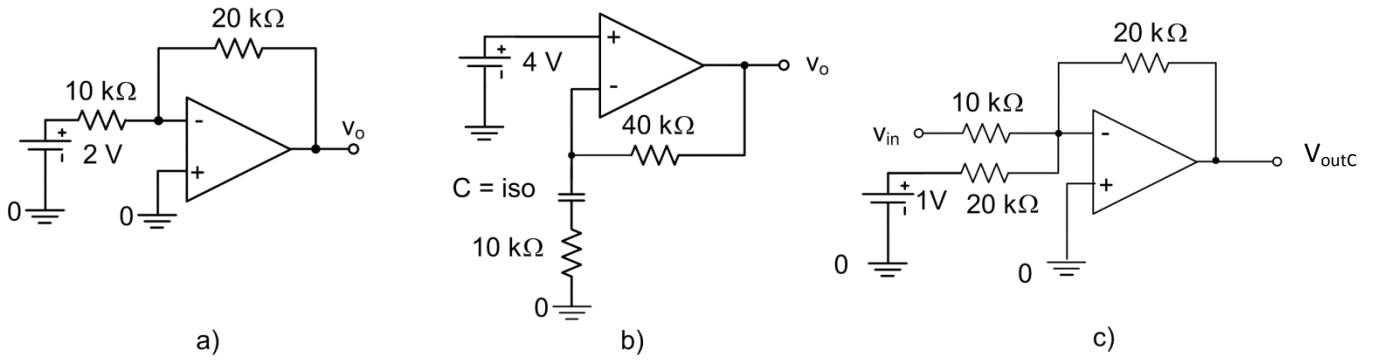


Figure 1.

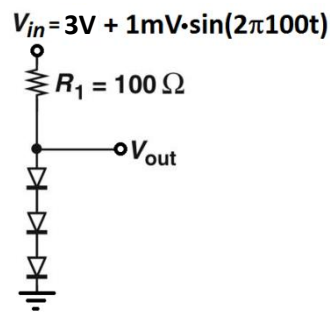


Figure 2.

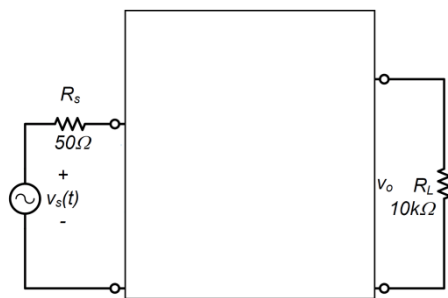


Figure 3.