

Circuit theory II 4.4.2003. (use of graphic calculators is allowed)

1. Define briefly the following terms:

- Stable network
- Amplitude and phase margin
- Lumped / distributed
- Causality
- Loop gain
- Nonlinear circuit

2. Derive the transfer function $U_o(s)/U_i(s)$ for fig. 1, draw the pole-zero map and draw the Bode plots. Is the network stable, and how did you verify it. Ratkaise kuvan 1 kytkennän siirtofunktio $U_o(s) / U_i(s)$, piirrä nolla-napa -kartta ja luonnostelee Bodein kuvaajat. Onko kytkentä stabiili, perustelee?

3. Calculate the z parameters for circuit in fig. 2

4. Calculate the v_o phasor in a steady state in fig. 3. $\omega = 10$ rad/s.

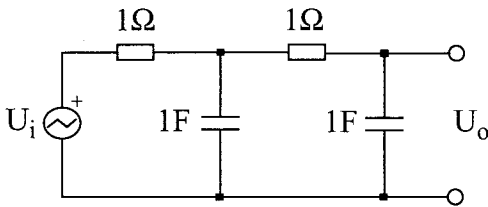


Fig 1

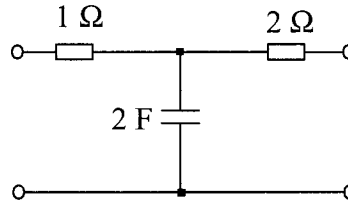


Fig 2

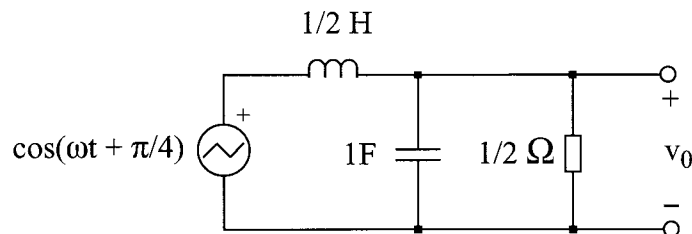


Fig 3