

Circuit Theory II (Graphical calculators are permitted)

1. Calculate the inverse Laplace-transformation to function $\frac{1}{(s^2 + 4s + 3)(s + 2)}$.
Use Table 1 for help.

2. $T(s)$ is the loop gain of an amplifier with negative feedback.

$$T(s) = \frac{10^{22}}{(s + 10^8)(s + 10^7)(s + 100)}$$

Construct a straight-line Bode amplitude and phase plot of $T(s)$. What are the gain and phase margins?

3. Calculate the voltage transfer function $V_2(s)/V_1(s)$ for the circuit shown in Fig.1.
Calculate voltage $v_2(t)$, when $t \geq 0$ and $v_1(t) = 10^{-9} \cdot \delta(t)$. No energy is stored in the circuit at $t = 0$.

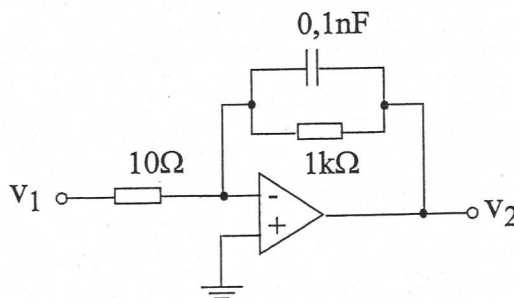


Fig 1.

4. Calculate the z-parameters for the 2-port shown in Fig. 2. Apply instructions shown in the next page.


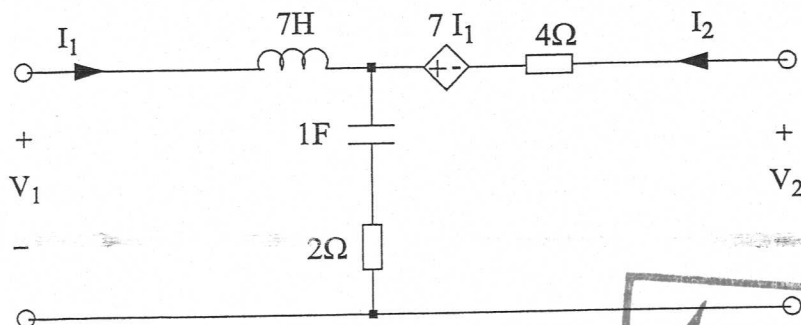


Fig. 2

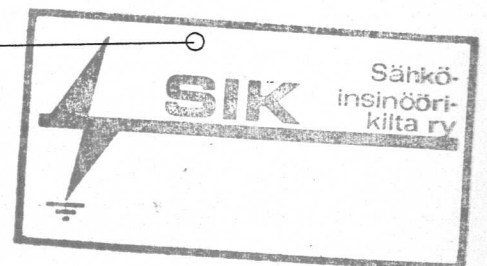

Circuit Theory II (Graphical calculators are permitted)

Table 1: Some Laplace-transform pairs

type	x(t)	X(s)
impulse	$\delta(t)$	1
unity-step u(t)	1	1 / s
exponential function	e^{-at}	1 / (s+a)
	$1 - e^{-at}$	a / (s(s+a))
	$t^n e^{-at}$	n! / (s+a)^{n+1}


z-parameters:

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

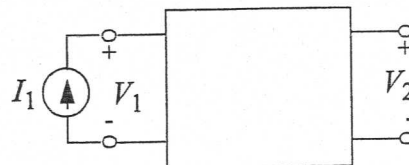

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

